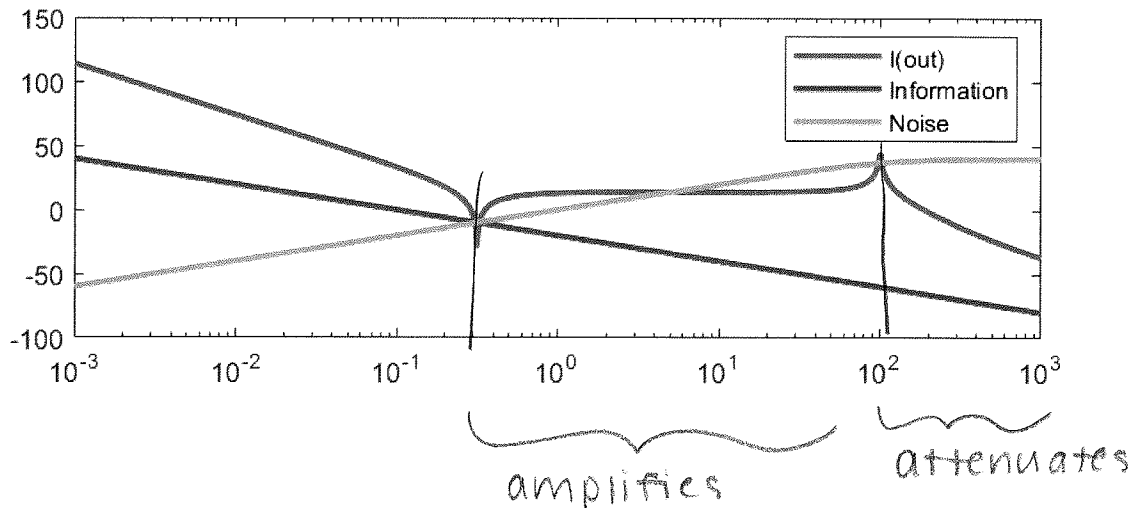


# Homework 11

## Problem 1

1.



2.

### Problem 2

$$Z_1 = 80 + j0 \Omega$$

$$Z_3 = 480 + j0 \Omega$$

$$C = 20 \text{ nF}$$


$$\omega_0 = 50 \text{ krad/sec}$$

$$|Q| = 6.25$$

$$1. \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{L(20 \cdot 10^{-9})}} = 50 \cdot 10^3$$

$$(2 \cdot 10^{-5}) = \sqrt{L(20 \cdot 10^{-9})}$$
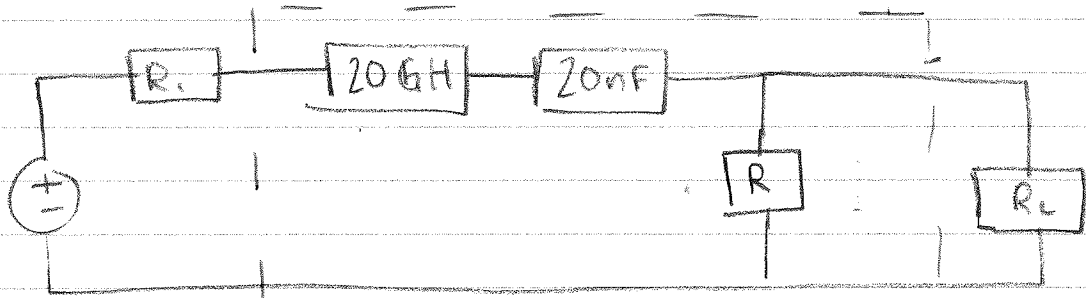
$$(4 \cdot 10^{-10}) = L(20 \cdot 10^{-9}) \quad L = 0.02$$



Filter

$$2. \quad \boxed{L = 20 \text{ mH}} \\ \boxed{C = 20 \text{ nF}}$$

$$BW = \frac{R}{L} \quad \text{connected system: } R_c = R_i + (R \parallel R_L)$$

$$Q = \frac{\omega_0}{BW} = \frac{50 \text{ krad/sec} \cdot (20 \cdot 10^{-3})}{R} = 6.25 \quad R = 160 \Omega$$

$$R_i = 80 \Omega$$

$$R = 160 \Omega$$

$$R_L = 480 \Omega$$

$$R_c = 80 + \left( \frac{1}{\frac{1}{160} + \frac{1}{480}} \right) = 80 + 120$$

$$R_c = 200 \Omega$$

3. Quality Factor

$$Q = \sqrt{\frac{L}{CR_c^2}} = \sqrt{\frac{(20 \cdot 10^{-3})}{(20 \cdot 10^{-9})(200)^2}} = \sqrt{2}$$

$$\boxed{Q=5}$$

4. Bandwidth

$$BW = \frac{R_c}{L} = \frac{200}{(20 \cdot 10^{-3})}$$

$$\boxed{BW=10000 \text{ Hz}}$$